


SUPERCONDUCTING QUBITS

- BASIS IN ELECTRIC CIRCUIT THEORY

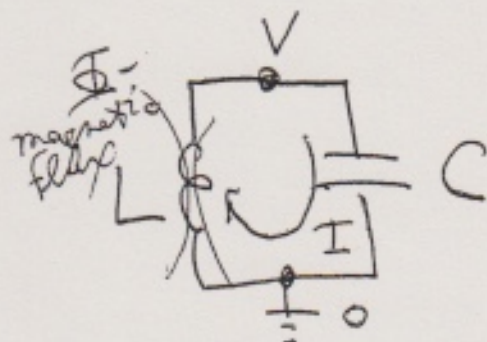1.

$$\Phi = -LI$$

$$\dot{\Phi} = V \quad (\text{Faraday})$$



$$(*) \quad Q = CV = C\dot{\Phi}$$

$$\dot{Q} = I = C\ddot{\Phi}$$

$$\Rightarrow \boxed{C\ddot{\Phi} = -\frac{1}{L}\Phi} \quad \text{equation of motion}$$

→ resonates @ $\omega_0 = \frac{1}{\sqrt{LC}}$

Lagrange function $\mathcal{L}(q, \dot{q})$
(conservative mechanics)

equation of motion from Lagrangian:

Euler-Lagrange equation:

$$\frac{d}{dt} \frac{\partial \mathcal{L}}{\partial \dot{q}} = \frac{\partial \mathcal{L}}{\partial q}$$

good guess

$$\mathcal{L} = \frac{1}{2}C(\dot{\Phi})^2 - \frac{1}{2L}\Phi^2$$

electric energy

magnetic energy

$$q \Leftrightarrow \Phi$$

↑
canonical coordinate

prescription for obtaining Hamiltonian function:

$$p \equiv \frac{\partial \mathcal{L}}{\partial \dot{q}} = \frac{\partial \mathcal{L}}{\partial \dot{\Phi}} = C\dot{\Phi}$$

C like a mass

Legendre transformation

$$H = \dot{q}p - \mathcal{L}, \text{ plus replace } \dot{q} = f(p)$$

$$\dot{\Phi} = \frac{1}{C}p$$

NB $p = Q$
from (*)


$$H = \frac{1}{2} C \dot{\Phi}^2 + \frac{1}{2L} \Phi^2$$

2.

$$H = \frac{Q^2}{2C} + \frac{1}{2L} \Phi^2$$

quantum postulate: $[\hat{Q}, \hat{\Phi}] = -i\hbar$
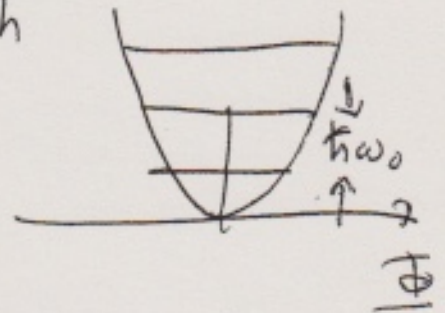
$$\hat{H} = \frac{-\hbar^2}{2C} \frac{\partial^2}{\partial \Phi^2} + \frac{1}{2L} \Phi^2$$



To make a qubit, make non-harmonic

⇒ nonlinear inductance

$$I = \frac{1}{L} \Phi \quad \text{linear}$$

= $f(\Phi)$ nonlinear → still non-dissipative

particular nonlinearity in superconducting tunneling device:

Josephson Junction:



$$I = \frac{\Phi_0}{L_J} \sin(\Phi / \Phi_0)$$

← "Josephson inductance"

$$\Phi_0 = \frac{h}{2e}$$

← usually just h .


$$\frac{\Phi_0}{L_J} = I_c \quad \text{critical current}$$

general theory for quantizing electric circuits:

Vool & Devoret

arXiv: 1610.03438

N^+ nodes

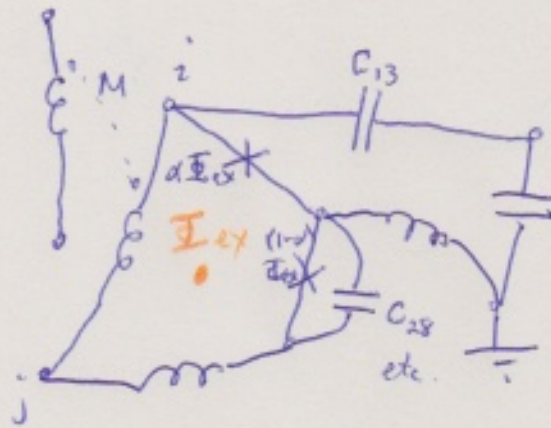

Pick one node, call it "ground": ($\Phi_{gr.} = 0$)

all other nodes (N): node fluxes Φ_i

NB $\dot{\Phi}_i = V_i$ more familiar node voltages.

Procedure:

1) Kinetic energies = capacitors.

$$T = \sum_{ij} \frac{1}{2} C_{ij} (\dot{\Phi}_i - \dot{\Phi}_j)^2 = \frac{1}{2} \dot{\Phi}^T C \dot{\Phi} = \frac{1}{2} \sum_{ij} C_{ij} \dot{\Phi}_i \dot{\Phi}_j$$

edges

nodes

can be = 0 (ground)

non-diagonal node matrix

e.g.

$$C = \begin{pmatrix} C_{13} & 0 & -C_{13} & & \\ 0 & 0 & 0 & & \\ -C_{13} & 0 & C_{13} & & \\ & & & \ddots & \\ & & & & \ddots \end{pmatrix} + \dots$$

2. potential energies:

a) individual ^{limit} inductances

$$U = \sum \frac{1}{2L_{ij}} (\Phi_i - \Phi_j)^2$$

susceptance = inverse inductance

b) coupled inductors:

$$\begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} L_1 & M \\ M & L_2 \end{pmatrix}^{-1} \begin{pmatrix} \Phi_1 \\ \Phi_2 \end{pmatrix}$$

M = mutual inductance

can be + or -


$$|M| \leq \sqrt{L_1 L_2} \text{ stability}$$

$$\begin{pmatrix} L_1 & M \\ M & L_2 \end{pmatrix}^{-1} \equiv \begin{pmatrix} S_{11} & S_{12} \\ S_{12} & S_{22} \end{pmatrix}$$


not tight coupled.

↳ tight coupling limit - special
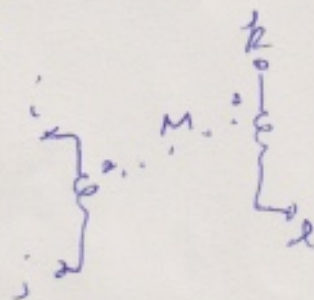
$$U = \frac{1}{2} S_{11} (\Phi_i - \Phi_j)^2 + S_{12} (\Phi_i - \Phi_j) (\Phi_k - \Phi_l) + \frac{1}{2} S_{22} (\Phi_k - \Phi_l)^2$$



c) tight coupling - special case:

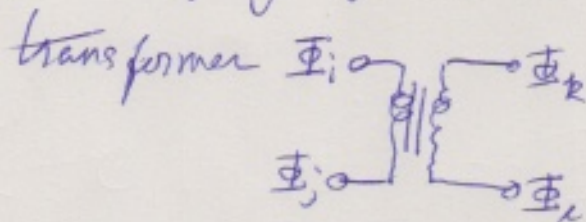

no potential energy contribution

Φ_k is not independent variable:

$$(\Phi_k - \Phi_l) = N(\Phi_i - \Phi_j)$$


N = turns ratio

$$\pm \sqrt{\frac{L_2}{L_1}} = N$$

comes from above with $M = \pm \sqrt{L_1 L_2}$, $L_1, L_2 \rightarrow \infty$,

d) ~~Josephson junction~~

~~with~~ voltage source

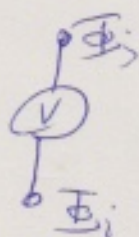

Φ_j not independent.

$$\Phi_j = \int V dt + \Phi_i$$

$$= Vt + \Phi_i \text{ for DC.}$$

can make L or H explicitly time dependent.

e) Josephson junctions:

nonlinear inductance:

$$U = \int_{-\infty}^t I_b(t') V_b(t') dt'$$

$\Phi_j = -\Phi_i$
↓
 $I_b(t') = f(\Phi_b(t'))$

general def. of inductance
NB t' same

J.J. $I_b = \frac{\Phi_0}{2\pi L_J} \sin\left(\frac{2\pi\Phi_b}{\Phi_0}\right)$
 I_c

$$\Phi_0 = \frac{h}{2e}$$

do integral:

$$U = \frac{\Phi_0^2}{(2\pi)^2 L_J} \cos\left(\frac{2\pi\Phi_b}{\Phi_0}\right)$$

E_J Josephson energy.

4. f) J.J.s with external fluxes:

gauge choice (see diagram) for inductor
only loops.

$$U = E_J \cos\left(\frac{2\pi}{\Phi_0} (\Phi_b - \alpha \Phi_{xy})\right)$$

∴

$$\mathcal{L} = T - U$$

$$= \frac{1}{2} \sum C_{ij} \dot{\Phi}_i \dot{\Phi}_j - U(\Phi)$$

[no V
branches]

Legendre transform:

$$\frac{\partial \mathcal{L}}{\partial \dot{\Phi}_i} = \sum_j C_{ij} \dot{\Phi}_j \equiv Q_i$$

($Q = CV$)
dimensionally correct.

$$H = \sum_i \dot{\Phi}_i Q_i - \mathcal{L}$$

$$= \frac{1}{2} \sum C_{ij} \dot{\Phi}_i \dot{\Phi}_j - \frac{1}{2} \sum C_{ij} \dot{\Phi}_i \dot{\Phi}_j + U(\Phi)$$

$$= + \frac{1}{2} \sum C_{ij} \dot{\Phi}_i \dot{\Phi}_j + U(\Phi)$$

$$= \frac{1}{2} \sum_j Q_j \dot{\Phi}_j + U(\Phi)$$

solve:

$$\dot{\Phi}_j = (C^{-1})_{ji} Q_i$$

$$H = \frac{1}{2} \sum_{ij} (C^{-1})_{ij} Q_i Q_j + U(\Phi)$$

if C is not invertible — start over! (add C_{loop})