
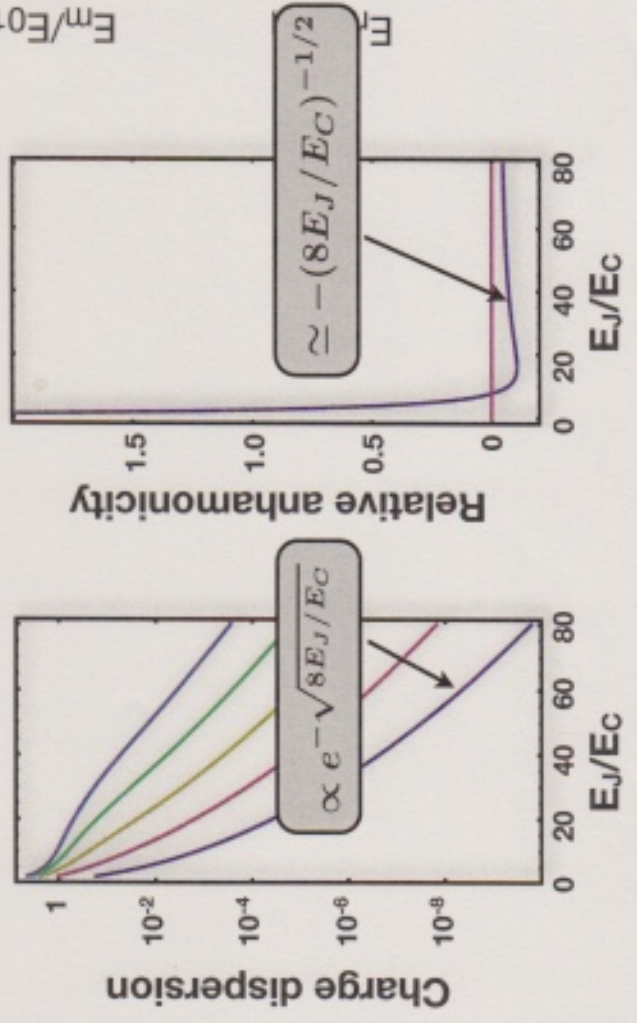
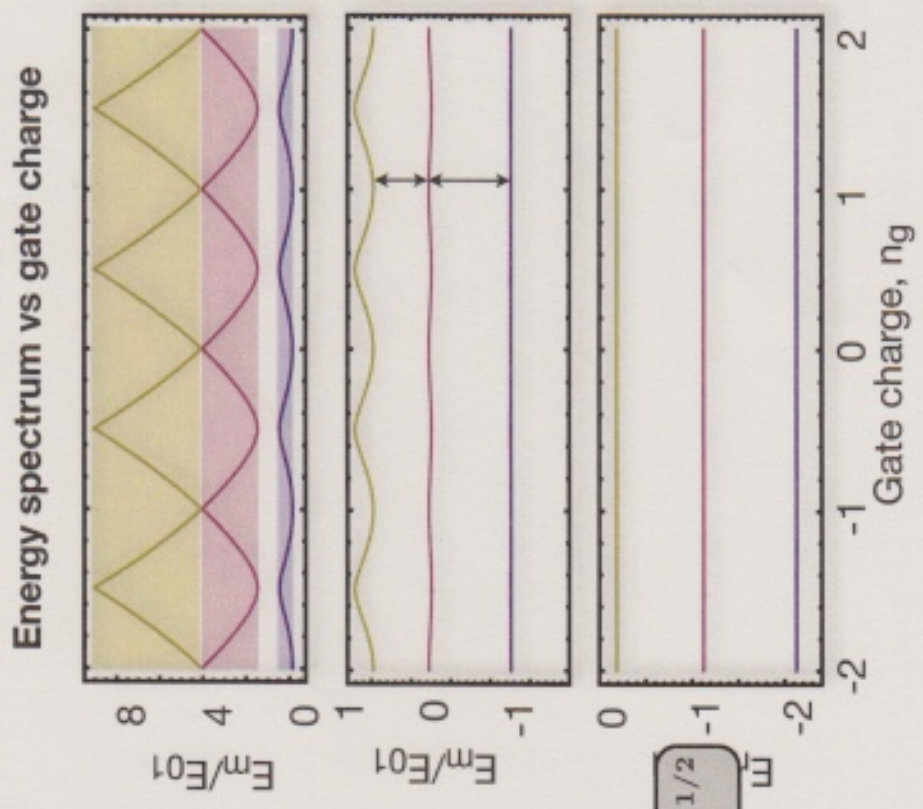


Superconducting qubit: transmon regime

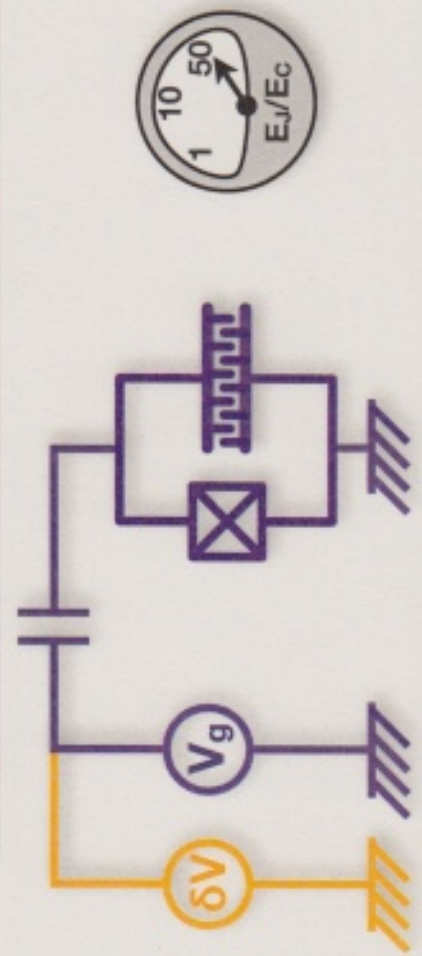


Transmon: J. Koch et al. Phys. Rev. A **76**, 042319 (2007)
 Sweet spot: D. Vion et al. Science **296**, 886 (2002)

Transmon regime: anharmonic oscillator


$$\begin{aligned}
 H &= 4E_C \hat{n}^2 - E_J \cos \hat{\phi} \\
 &\approx 4E_C \hat{n}^2 + \frac{1}{2} E_J \hat{\phi}^2 - \frac{1}{24} E_J \hat{\phi}^4 \\
 &\equiv \frac{\hat{n}^2}{2C''} + \frac{\hat{\phi}^2}{2L'} - \frac{1}{24} E_J \hat{\phi}^4
 \end{aligned}$$

$$\begin{aligned}
 \hat{n} &= i\sqrt{\hbar} \left(\frac{E_J}{32E_C} \right)^{1/4} (\hat{b}^\dagger - \hat{b}) \\
 \hat{\phi} &= \sqrt{\hbar} \left(\frac{2E_C}{E_J} \right)^{1/4} (\hat{b}^\dagger + \hat{b})
 \end{aligned}$$

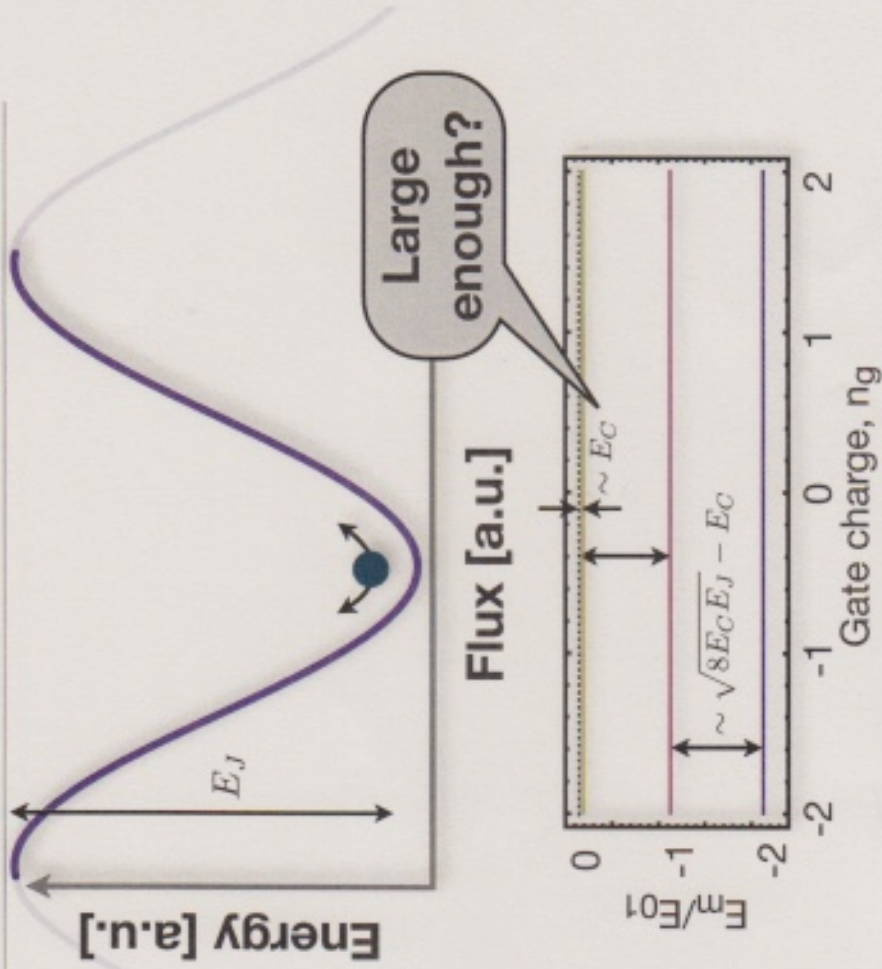
$$\begin{aligned}
 H &\approx \sqrt{8E_C E_J} \hat{b}^\dagger \hat{b} - \frac{E_C}{2} (\hat{b}^\dagger \hat{b}^\dagger \hat{b} \hat{b} + 2\hat{b}^\dagger \hat{b}) \\
 &= (\sqrt{8E_C E_J} - E_C) \hat{b}^\dagger \hat{b} - \frac{E_C}{2} \hat{b}^\dagger \hat{b}^\dagger \hat{b} \hat{b}
 \end{aligned}$$



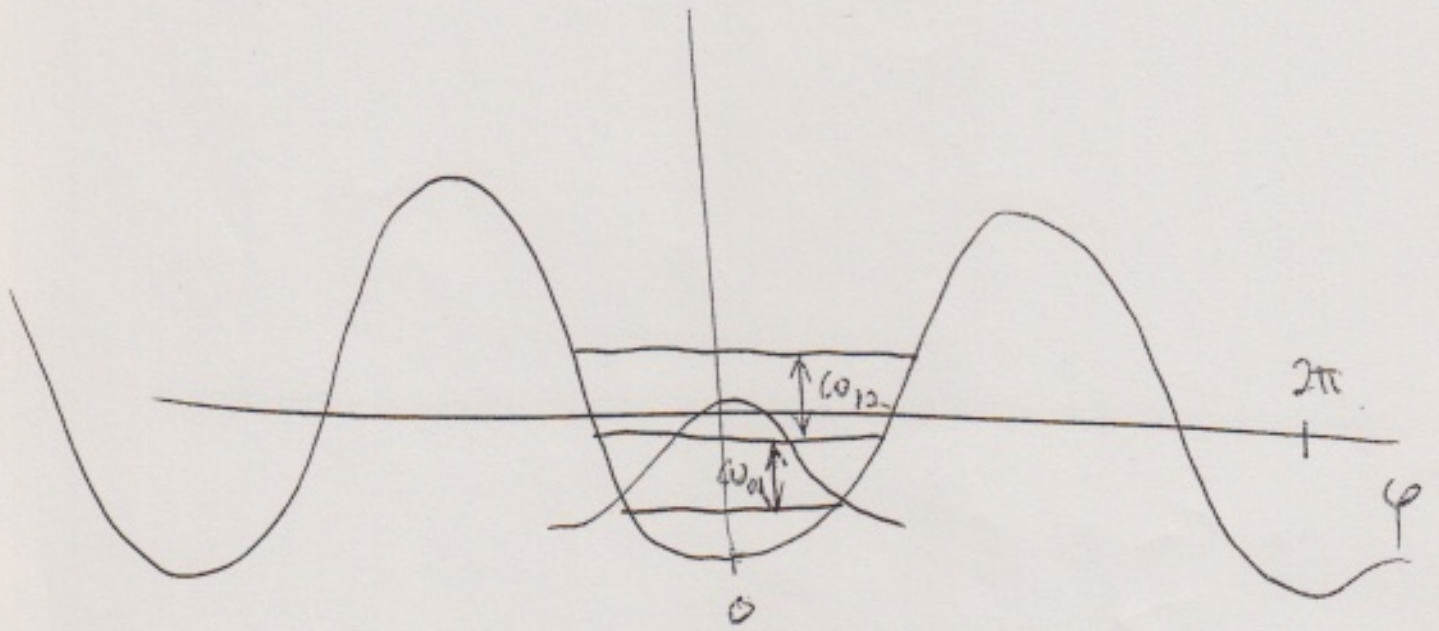
Typical values:
 $E_J \sim 20$ GHz
 $E_C \sim 400$ MHz



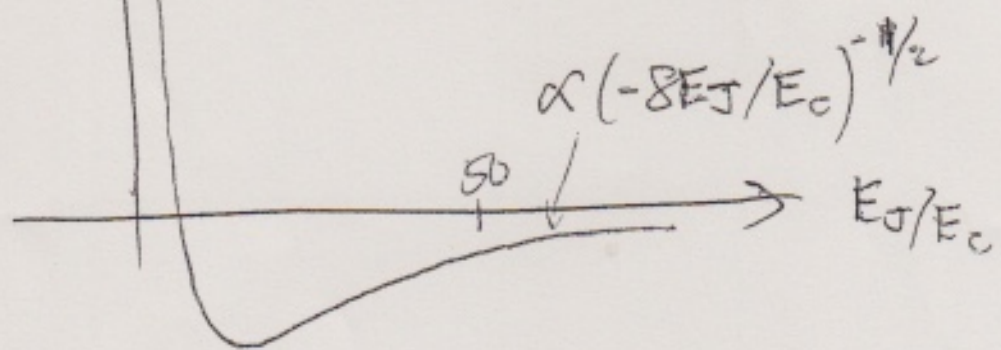
anharmonicity
 $\omega_{12} - \omega_{01}$



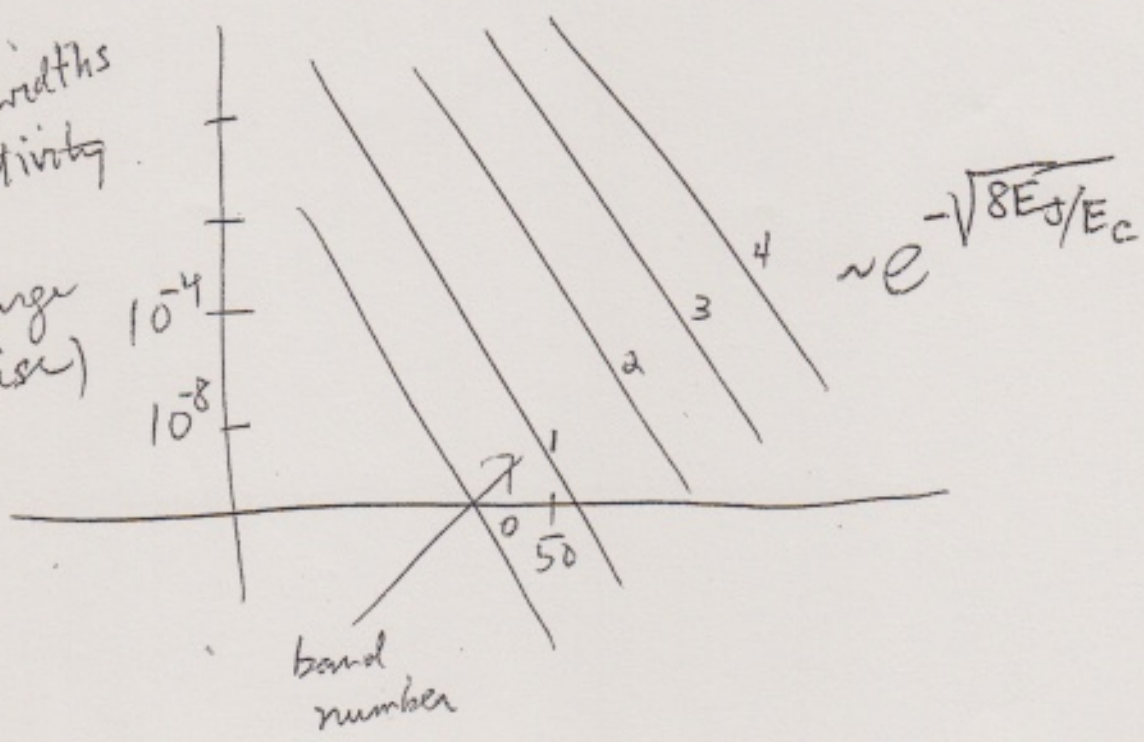bandwidths
 (sensitivity
 to
 charge
 noise)



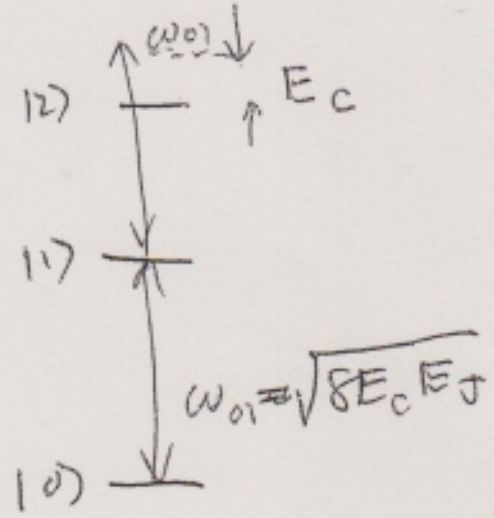H_0 i.e., charge sensitivity exponentially suppressed, anharmonicity "reasonable".




- Very accurate 1-qubit gates,

$$F = 99.993\%$$

- COUPLING TRANSMONS.

coplanar waveguide:

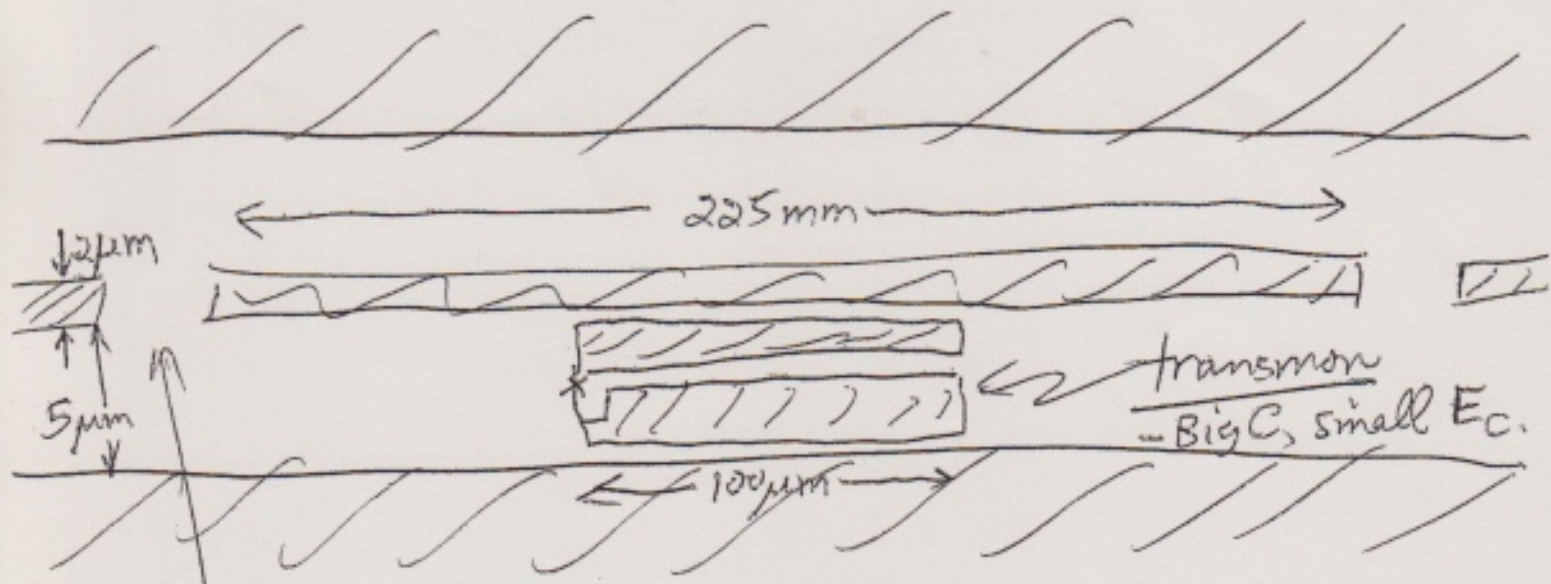


coupling capacitors C_{coup} .

→ slightly transparent mirror for microwaves

CPW is cavity for microwave photons, $\frac{\omega_c}{2\pi} = 2-20$ GHz.

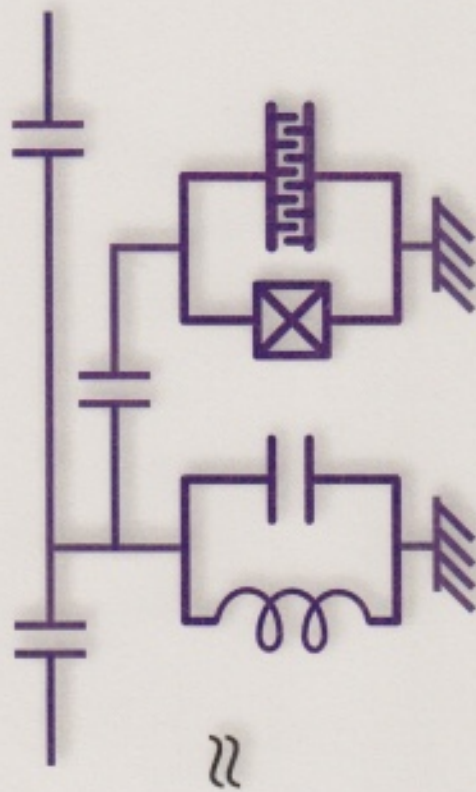Bringing it all together: Jaynes-Cummings model



$$\hat{H} = \left(\frac{\hat{Q}_r^2}{2C_r} + \frac{\hat{\Phi}_r^2}{2L_r} \right) + (4E_C [\hat{n} - \hat{n}_r]^2 - E_J \cos \hat{\phi})$$

$$= \omega_r \hat{a}^\dagger \hat{a} + \left(\omega_{01} \hat{b}^\dagger \hat{b} - \frac{E_c}{2} \hat{b}^\dagger \hat{b} \hat{b} \right) - g(\hat{a}^\dagger - \hat{a})(\hat{b}^\dagger - \hat{b})$$

TLS
approx.

$$= \omega_r \hat{a}^\dagger \hat{a} + \frac{\omega_{01}}{2} \hat{\sigma}_z - g(\hat{a}^\dagger - \hat{a})(\hat{\sigma}_+ - \hat{\sigma}_-)$$

$$\approx \omega_r \hat{a}^\dagger \hat{a} + \frac{\omega_{01}}{2} \hat{\sigma}_z + g(\hat{a}^\dagger \hat{\sigma}_- + \hat{a} \hat{\sigma}_+)$$

RWA

Energy exchange between
'light' and 'matter' at rate $2g$

$$g_{\text{circuit}}/2\pi \sim [0 - 1] \text{ GHz}$$

$$g_{\text{cavity}}/2\pi \sim 50 \text{ kHz}$$

calculate Jaynes Cummings coupling g :

$$8E_c \hat{n} \hat{n}_r = \frac{8E_c}{(2e)^2} \hat{Q} \hat{Q}_r$$

$$\frac{\hat{Q}}{2e} = i \left(\frac{E_J}{32E_c} \right)^{1/4} (b^\dagger - b)$$

$$\frac{\hat{Q}_r}{2e} = i \left(\frac{E_{Jr}}{32E_{cr}} \right)^{1/4} (a^\dagger - a)$$


coupling = - ~~$A A E$~~ $E_{c \text{ tot}}$

\downarrow
 e^2
 C

$g = E_{\text{coup}} \left(\frac{E_J}{32E_c} \right)^{1/4} \left(\frac{E_{Jr}}{32E_{cr}} \right)^{1/4}$

$\propto C_g$

start over:

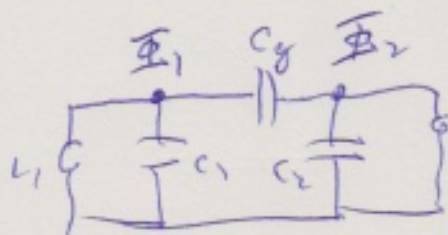

$$C_{\text{node}} = \begin{pmatrix} C_1 + C_g & -C_g \\ -C_g & C_2 + C_g \end{pmatrix}$$

in N , coupling term is $(C_g \ll C_1, C_2)$:



$$E_{\text{coup}} \hat{n} \hat{n}_r = \frac{\hat{Q}_1 \hat{Q}_2 C_g}{C_1 C_2}$$

$$E_{\text{coup}} = \frac{(2e)^2 C_g}{C_1 C_2}$$


Dispersive regime: Qubit readout $|\Delta| = |\omega_{01} - \omega_r| \gg g$

Dispersive interaction: $H \approx (\omega_r + \chi \hat{\sigma}_z) \hat{a}^\dagger \hat{a} + \frac{\tilde{\omega}_{01}}{2} \hat{\sigma}_z$

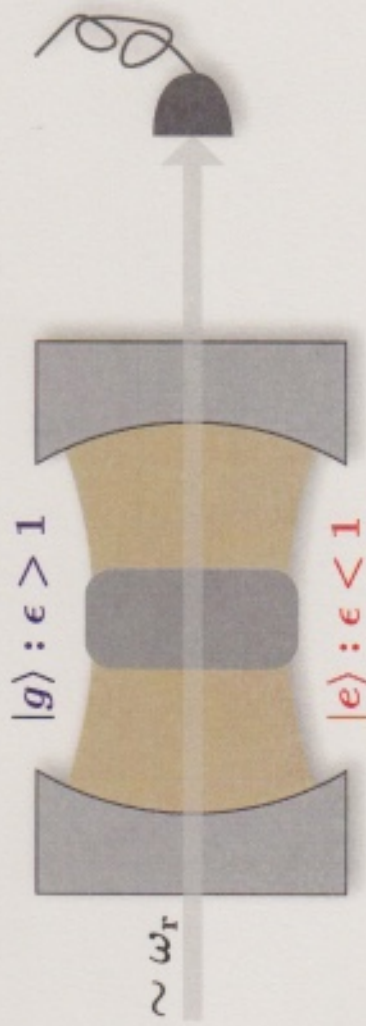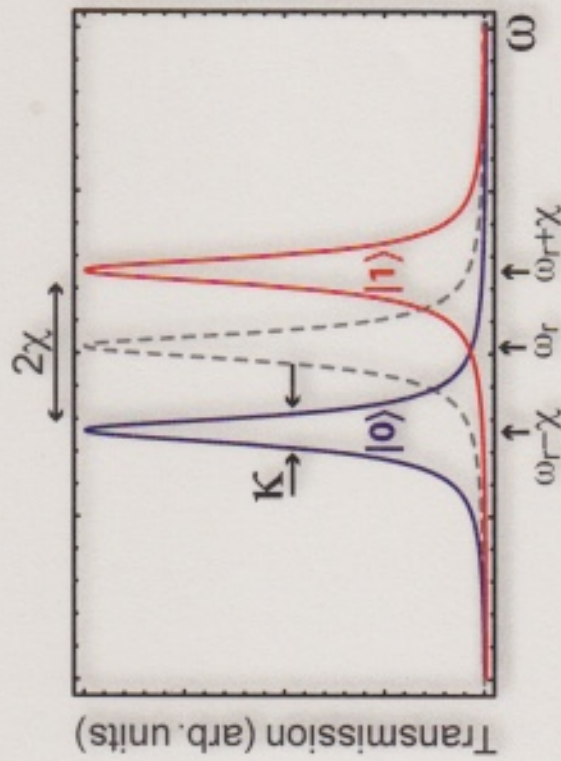ω_r Resonator frequency
 $\chi = g^2 / \Delta$ Dispersive interaction strength
 $\tilde{\omega}_{01}$ Qubit transition frequency



I. Circuit model:

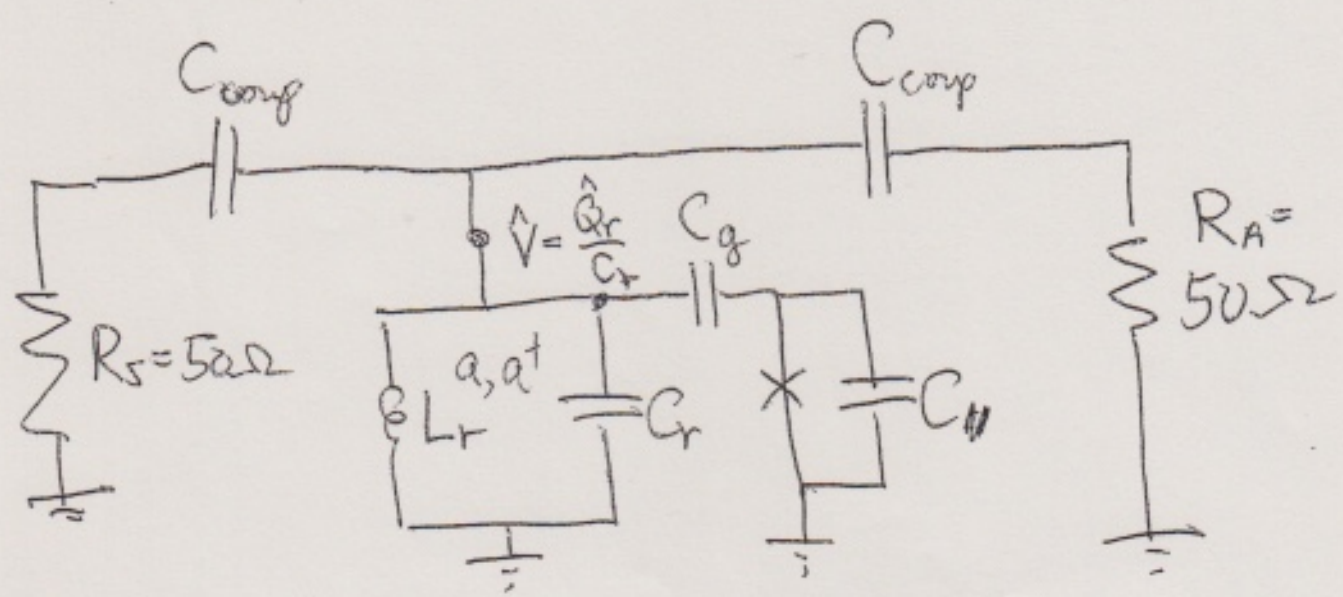

R_S, R_A : source & amplifier impedances

L_r, C_r : model for first resonant mode of transmission line resonator

circuit Hamiltonian

$$H = \frac{\hat{Q}_r^2}{2C_r} + \frac{\Phi_r^2}{2L_r} + [4E_c (\hat{n} - \hat{n}_{offset})^2 - E_J \cos \hat{\varphi}]$$

$$\hat{n}_{offset} = \frac{C_g}{2e} \hat{V} = \frac{C_g}{2eC_r} \hat{Q}_r \leftarrow \text{offset-charge operator}$$

coupling term $-8E_c \hat{n} \hat{n}_{offset}$
 2nd quantize:


rotating-wave approx.

$$H = \omega_r a^\dagger a + \frac{\omega_J}{2} Z + g (a^\dagger \sigma_- + a \sigma_+)$$


Jaynes-Cummings model:

So, we come to what is
 needed: ^{the} connection

Gyrator: (Tellegen 1948)

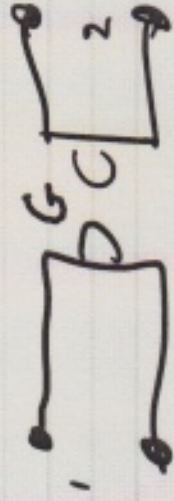

(circulator is
 Hoogen (1952))

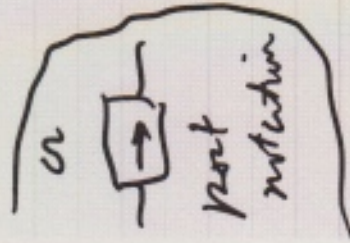

$$I_1 = GV_2$$

$$I_2 = GV_1$$

$$Y_{port} = \begin{pmatrix} 0 & -G \\ +G & 0 \end{pmatrix}$$

$$\text{if } G = \frac{1}{Z_0} : S_{port} = \begin{pmatrix} 0 & -1 \\ +1 & 0 \end{pmatrix}$$

- Tellegen said that gyration is lossless.
- Lagrangian. We will explore

$$L_{\text{gyrator}} = \frac{1}{2} G \left[(1+k) \dot{\Phi}_1 \dot{\Phi}_2 - (1-k) \dot{\Phi}_2 \dot{\Phi}_1 \right]$$

consider circuit



full Lagrangian: current source

$$L = \frac{1}{2} G \left[(1+k) \dot{\Phi}_2 - (1-k) \dot{\Phi}_1 \right]^2 + I \dot{\Phi}_1$$

$$\frac{\partial L}{\partial \dot{\Phi}_2} = \frac{1}{2} (1-k) G \dot{\Phi}_1 \quad \frac{\partial L}{\partial \dot{\Phi}_1} = \frac{1}{2} (1+k) G \dot{\Phi}_2 + I$$

$$\frac{\partial L}{\partial \Phi_1} = \frac{1}{2} (1+k) G \dot{\Phi}_2 - I \quad \frac{\partial L}{\partial \Phi_2} = -\frac{1}{2} (1-k) G \dot{\Phi}_1$$

$$\dot{\Phi}_1 = 0 \Rightarrow V_1 = 0$$

$$\dot{\Phi}_2 = \frac{I}{G} \Rightarrow V_2 = -\frac{I}{G}$$

we would find:

$$V_2 = -\frac{1}{G} I_1$$

$$V_1 = +\frac{1}{G} I_2 \quad (\text{current source } \odot 2)$$


$$Z = \begin{pmatrix} 0 & \frac{1}{G} \\ -\frac{1}{G} & 0 \end{pmatrix} = Y_{\text{gyrator}}^{-1} \quad \checkmark$$

• NB: independent of K !


K is a gauge degree of freedom.

Tellegen said gyrator does not store energy, but it does have a term in the Lagrangian.

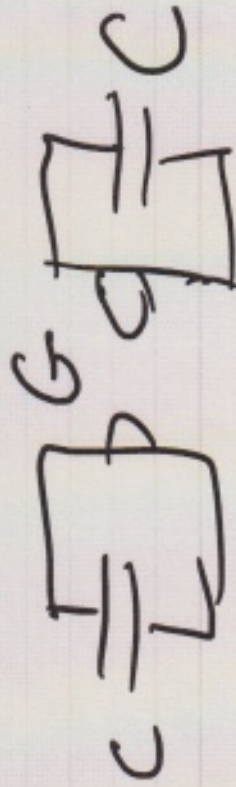Interpretation of this is given by final example:



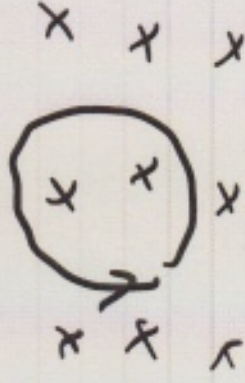
doing the Euler-Lagrange equations (homework), we get the equations of motion of a charged particle in 2D, with mass m , in a uniform magnetic field $\propto G$



solution - cyclotron motion,
frequency is

$$\omega = \frac{G}{C}$$

explained by electrical engineers
with identity
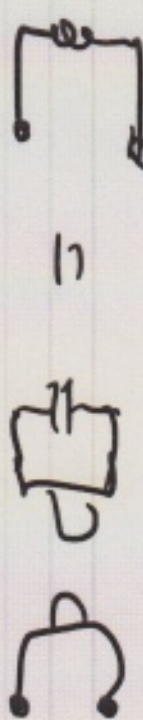
$$\omega = \frac{1}{\sqrt{LC}} \quad \omega = \frac{G}{C}$$

$$L = \frac{1}{G^2 C}$$